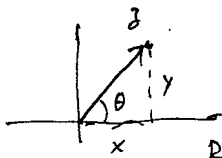


# Basics of Complex numbers

The complex number  $z = x + jy$  can be represented by the point  $(x, y)$  on the  $x$ - $y$  plane, or the vector from  $(0, 0)$  to  $(x, y)$



$$|z| = \sqrt{x^2 + y^2} \quad \text{is called its magnitude}$$

$$\theta = \tan^{-1} \frac{y}{x} \quad \text{is called its argument}$$

Real part of  $z$  is  $x$ , imaginary part of  $z$  is  $y$



Operations with complex numbers follow the rule of ~~arithmetic~~ algebra with the proviso that  $j^2 = -1$ .

Examples ①  $(2 + 3j)(1 - j) = 2 - 2j + 3j + 3j(-j) = 2 + j + 3 = 5 + j$

②  $\frac{2 + 3j}{1 - 2j} = \frac{(2 + 3j)(1 + 2j)}{(1 - 2j)(1 + 2j)} = \frac{2 + 4j + 3j - 6}{1 + 4} = -\frac{4}{5} + \frac{7}{5}j$

③  $j = -j$

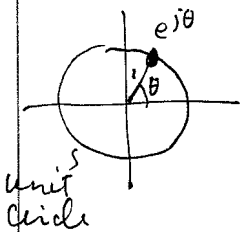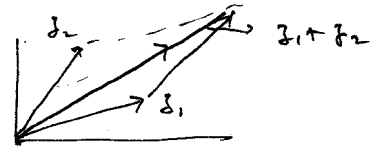Addition of ~~two~~ complex numbers can be interpreted as vector addition on the complex plane:



$$e^{j\theta} = \cos\theta + j\sin\theta$$

$$e^{j\theta_1} \cdot e^{j\theta_2} = (\cos\theta_1 + j\sin\theta_1)(\cos\theta_2 + j\sin\theta_2)$$

$$= (\cos\theta_1 \cos\theta_2 - \sin\theta_1 \sin\theta_2) + j(\sin\theta_1 \cos\theta_2 + \cos\theta_1 \sin\theta_2)$$

$$= \cos(\theta_1 + \theta_2) + j\sin(\theta_1 + \theta_2) = e^{j(\theta_1 + \theta_2)}$$

$\therefore e^{j\theta}$  behaves like exponential function

$$e^{-j\theta} = \frac{1}{e^{j\theta}}$$

$$\frac{d}{d\theta} e^{j\theta} = j e^{j\theta}$$

$$\frac{d}{dt} e^{j\omega t} = j\omega e^{j\omega t}$$


A complex number  $z = x + jy$  can be written in the polar form

$$z = A e^{j\theta} \quad A = \sqrt{x^2 + y^2} = |z|, \quad \theta = \tan^{-1} \frac{y}{x}$$

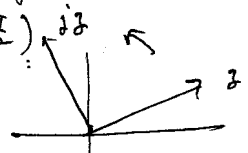Examples ①  $2 - 3j = \sqrt{2^2 + 3^2} e^{-j\phi} = 3.6 e^{-0.98j}$   $\phi = \tan^{-1} \frac{3}{2} = 0.98 \text{ rad.}$

②  $j = e^{j\frac{\pi}{2}} \quad -j = e^{-j\frac{\pi}{2}}$

Multiplication of a complex number by  $j$  corresponds to rotation by  $90^\circ$ :  $jz = e^{j\frac{\pi}{2}} A e^{j\theta} = A e^{j(\theta + \frac{\pi}{2})}$



If  $z_1 = A_1 e^{j\theta_1}$ ,  $z_2 = A_2 e^{j\theta_2}$

$$z_1 z_2 = A_1 A_2 e^{j(\theta_1 + \theta_2)} \quad \frac{z_1}{z_2} = \frac{A_1}{A_2} e^{j(\theta_1 - \theta_2)}$$

# Use of Complex numbers in AC Circuits

Any sinusoidally oscillating quantity

$$A = A_{max} \cos(\omega t + \phi) = \text{real part of } A_{max} e^{j(\omega t + \phi)}$$


$$= \text{Re} [A_{max} e^{j\phi} \cdot e^{j\omega t}] = \text{Re} (a e^{j\omega t})$$

where  $a = A_{max} e^{j\phi}$  will be used to represent  $A$ .

To recover  $A$  from  $a$ , just take the real part of  $a e^{j\omega t}$
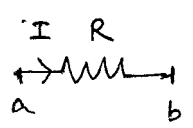
## Complex voltage-current relations


$$I = I_{max} \cos(\omega t + \phi) \rightarrow i = I_{max} e^{j\phi}$$



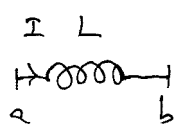(1) Resistor

$$V = V_a - V_b = RI = R I_{max} \cos(\omega t + \phi) = \text{Re} [R I_{max} e^{j\phi} \cdot e^{j\omega t}]$$

$$= \text{Re} \left[ \frac{R i}{v} e^{j\omega t} \right] \quad \therefore v = R i$$




(2) Inductance

$$V = L \frac{dI}{dt} = -\omega L I_{max} \sin(\omega t + \phi) = \omega L I_{max} \cos(\omega t + \phi + \frac{\pi}{2})$$

$$= \text{Re} [\omega L I_{max} e^{j(\phi + \frac{\pi}{2})} e^{j\omega t}] = \text{Re} [\omega L I_{max} e^{j\phi} \cdot e^{j\frac{\pi}{2}} \cdot e^{j\omega t}]$$

$$= \text{Re} [\omega L e^{j\frac{\pi}{2}} \cdot I_{max} e^{j\phi} \cdot e^{j\omega t}]$$
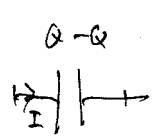
$$= \text{Re} \left[ \frac{j\omega L \cdot i}{v} e^{j\omega t} \right] \quad \therefore v = j\omega L i$$



(3) Capacitor

$$V = \frac{Q}{C} = \frac{1}{C} \int I dt = \frac{1}{\omega C} I_{max} \sin(\omega t + \phi)$$

$$= \frac{1}{\omega C} I_{max} \cos(\omega t + \phi - \frac{\pi}{2}) = \text{Re} \left[ \frac{1}{\omega C} I_{max} e^{j(\phi - \frac{\pi}{2})} e^{j\omega t} \right]$$


$$= \text{Re} \left[ \frac{1}{j\omega C} \cdot i \cdot e^{j\omega t} \right] \quad v = \frac{1}{j\omega C} i$$

Thus, in general,  $v = z i$  where

	Resistor	Inductor	Capacitor
$z$	$R$	$j\omega L$	$\frac{1}{j\omega C}$

Instead of using lower case  $v, z, i$ , we can use  $V, Z, I$  with the understanding that real parts are to be taken at the end.

Impedance in series

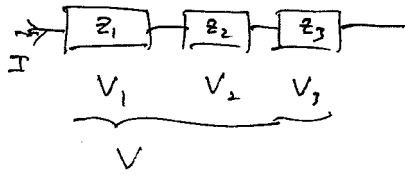

$$V_1 = IZ_1$$


$$V_2 = IZ_2$$

$$V_3 = IZ_3$$

$$\therefore V = V_1 + V_2 + V_3 = I(Z_1 + Z_2 + Z_3) = IZ$$

$$Z = Z_1 + Z_2 + Z_3$$

Impedance in parallel

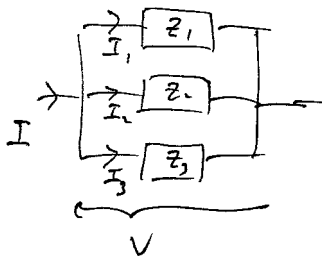


$$I_1 = \frac{V}{Z_1} \quad I_2 = \frac{V}{Z_2} \quad I_3 = \frac{V}{Z_3}$$

$$I = I_1 + I_2 + I_3 = V \left( \frac{1}{Z_1} + \frac{1}{Z_2} + \frac{1}{Z_3} \right) = \frac{V}{Z}$$

$$\frac{1}{Z} = \frac{1}{Z_1} + \frac{1}{Z_2} + \frac{1}{Z_3}$$

Example 1 RLC circuit

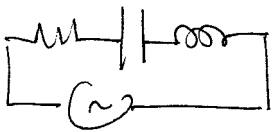


$$\mathcal{E} = \mathcal{E}_{\max} \cos \omega t = \operatorname{Re} \left( \frac{\mathcal{E}_{\max}}{\mathcal{E}} e^{j\omega t} \right)$$

$$Z = R + j\omega L + \frac{1}{j\omega C} = R + j \left( \omega L - \frac{1}{\omega C} \right)$$

$$I = \frac{\mathcal{E}}{Z}$$

In polar form  $Z = \sqrt{R^2 + \left( \omega L - \frac{1}{\omega C} \right)^2} e^{j\phi}$

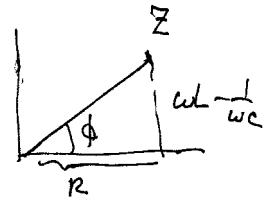
$$\tan \phi = \frac{\omega L - \frac{1}{\omega C}}{R}$$



$$\therefore I = \frac{\mathcal{E}}{\sqrt{R^2 + \left( \omega L - \frac{1}{\omega C} \right)^2}} e^{-j\phi}$$

Actual current =  $\frac{\mathcal{E}_{\max}}{\sqrt{R^2 + \left( \omega L - \frac{1}{\omega C} \right)^2}} \cos(\omega t - \phi)$

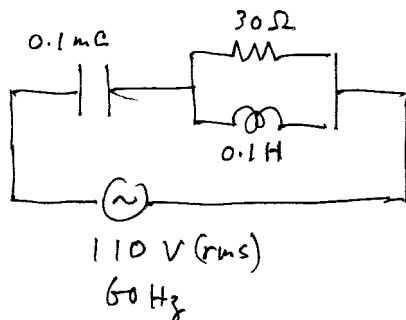Example 2. Find  $I_{rms}$  and power delivered by generator in the circuit



$$\omega = 2\pi \times 60 = 377 \text{ rad/s}$$

Equivalent impedance of  $30\Omega + 0.1\text{H}$  in parallel is given by


$$\frac{1}{Z_2} = \frac{1}{R} + \frac{1}{j\omega L} = \frac{j\omega L + R}{j\omega L R} = \frac{jX_L + R}{jX_L R}$$

$$\therefore Z_2 = \frac{jX_L R}{R + jX_L}$$

$$X_L = \omega L = 377 \times 0.1 = 37.7\Omega$$

$$= \frac{jX_L R (R - jX_L)}{(R + jX_L)(R - jX_L)} = \frac{jX_L R^2 + X_L^2 R}{R^2 + X_L^2} = \frac{RX_L}{R^2 + X_L^2} (X_L + jR)$$


$$= 18.4 + 14.6j$$

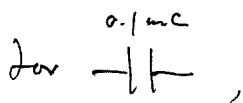

$$\ominus Z_1 = \frac{1}{j\omega C} = -\frac{j}{\omega C} = -26.5j$$

$\therefore$  Equivalent impedance of circuit is

$$Z = Z_1 + Z_2 = 18.4 - 11.9j = |Z| e^{-j\delta}$$

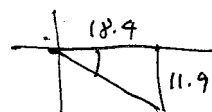

$$|Z| = \sqrt{18.4^2 + 11.9^2} = 21.9\Omega$$

$$\delta = \tan^{-1} \frac{11.9}{18.4} = 32.9^\circ = 0.584 \text{ rad}$$

$$I = \frac{E}{Z} = \frac{E}{|Z| e^{-j\delta}} = \frac{E}{|Z|} e^{j\delta} = \frac{110}{21.9} e^{j\delta} = 5.02 e^{j\delta}$$

$$\therefore I_{rms} = 5.02 \text{ A}$$


$$I_{max} = \sqrt{2} I_{rms} = 7.10 \text{ A}$$

Real current is  $I = 7.10 \cos(\omega t + \delta) = I_{max} \cos(\omega t + \delta)$

Power delivered by generator is

$$\langle EI \rangle = E_{rms} I_{rms} \cos \delta = 110 \times 5.02 \times \cos 32.9^\circ = 464 \text{ W}$$

Example 3 RLC circuit without generator

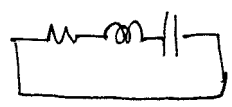

from  $\mathcal{E} = IZ$  follows  $Z=0$  if  $\mathcal{E}=0$

$R + j\omega L + \frac{1}{j\omega C} = 0$  is an equation for  $\omega$ .

$j\omega CR - \omega^2 LC + 1 = 0$   
 $\omega^2 - \frac{jR}{L}\omega - \frac{1}{LC} = 0$

$\omega = + \frac{jR}{2L} \pm \sqrt{\left(-\frac{jR}{2L}\right)^2 + \frac{1}{LC}} = \pm \sqrt{\frac{1}{LC} - \frac{R^2}{4L^2}} + j \frac{R}{2L}$


Case 1  $\frac{1}{LC} > \frac{R^2}{4L^2}$  (underdamped)

$\omega_0 = \sqrt{\frac{1}{LC} - \frac{R^2}{4L^2}}$  is a real number

$I = I_{max} e^{j\omega t} = I_{max} e^{j(\pm\omega_0 + j\frac{R}{2L})t} = I_{max} e^{-\frac{R}{2L}t} \cdot e^{\pm j\omega_0 t}$

Real part of  $I$  is  $I_{max} e^{-\frac{R}{2L}t} \cos(\omega_0 t)$

which is a damped oscillation

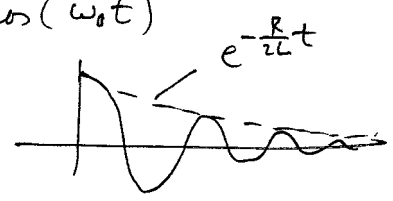


Case 2  $\frac{1}{LC} < \frac{R^2}{4L^2}$  (over damped)

$\sqrt{\frac{1}{LC} - \frac{R^2}{4L^2}} = \sqrt{\left(\frac{R^2}{4L^2} - \frac{1}{LC}\right)(-1)} = \sqrt{\frac{R^2}{4L^2} - \frac{1}{LC}} \cdot j$   $j = \sqrt{-1}$

$\therefore \omega = j \left[ \frac{R}{2L} \pm \sqrt{\frac{R^2}{4L^2} - \frac{1}{LC}} \right] = j\gamma_1, j\gamma_2$  two solutions  $\gamma_1, \gamma_2 > 0$

$\therefore I = I_{max} e^{j\omega t} = I_{max} e^{-\gamma_1 t}$  or  $I_{max} e^{-\gamma_2 t}$

or any combination  $I$

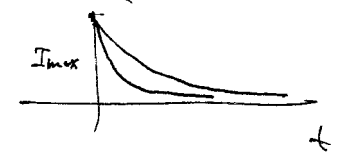

Case 3  $\frac{1}{LC} = \frac{R^2}{4L^2}$  (critically damped)

$\omega = j \frac{R}{2L}$

$I = I_{max} e^{-\frac{R}{2L}t}$